

About the voltage of the Function Generator

The function generator outputs the original signal voltage "V(=2×Vs)" on the premise of 50Ω termination.

The voltage $V_r[V]$ applied to the load impedance $R[\Omega]$ is obtained as follows when the output voltage set to $V_s[V]$.

$$V_r [V] = 2 \times V_s [V] \times \frac{R[\Omega]}{(50[\Omega] + R[\Omega])}$$

- When Load $R = 50\Omega$, Setting Voltage: $V_s = 10V_{pp}$

$$V_r[V_{pp}] = 2 \times 10[V_{pp}] \times 50[\Omega] / (50[\Omega] + 50[\Omega]) = 10[V_{pp}]$$

- When Load $R = 1M\Omega$, $V_s = 10V_{pp}$

$$V_r[V_{pp}] = 2 \times 10[V_{pp}] \times 1M[\Omega] / (50[\Omega] + 1M[\Omega]) \approx 20[V_{pp}]$$

50Ω Load


Function Generator



AFG series: 1 mV_{pp} to 10 V_{pp} (into 50Ω)

Open circuit


Function Generator

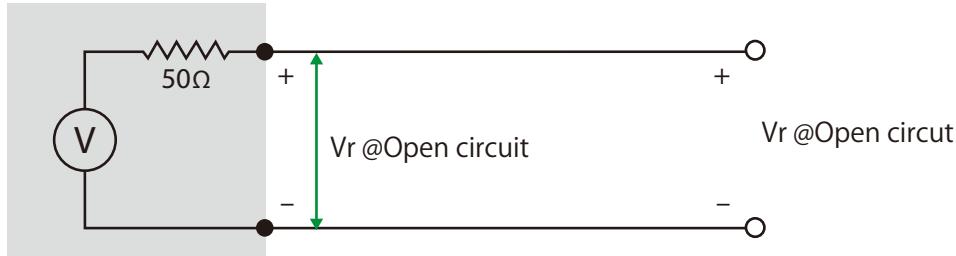

$V_r @ 50\Omega \times 2 = V_r @ Open Circuit$

1MΩ

Function Generator

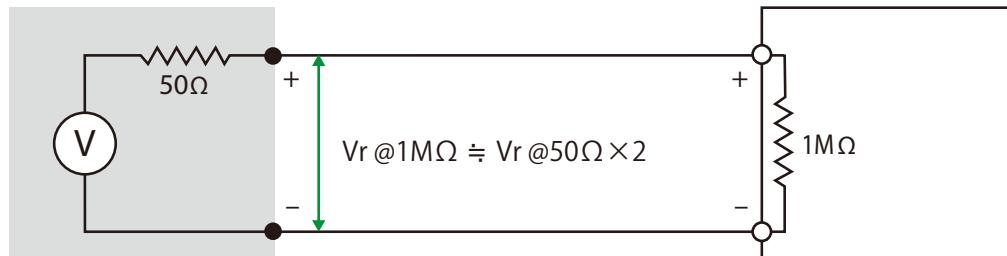

AFG series: 2 mV_{pp} to 20 V_{pp} (@1MΩ)